

# Programming Logic

## Lesson 1

1. Fill the tables with the correct answers.

a. NOT

A	$\bar{A}$

b. AND

A	B	$A \wedge B$

c. OR

A	B	$A \vee B$

d. XOR

A	B	A XOR B

2. Give the correct A, B, C, D and E to turn on the lamp.

